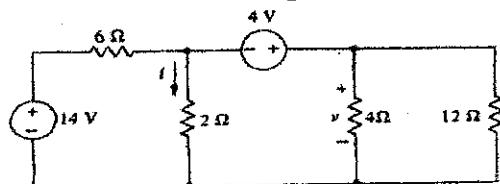
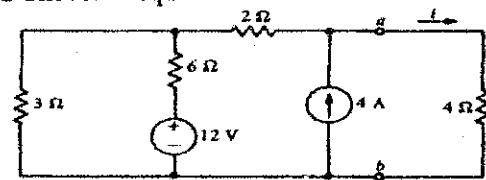
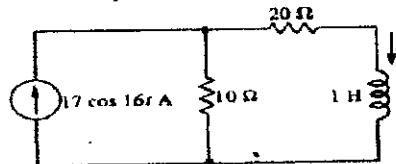
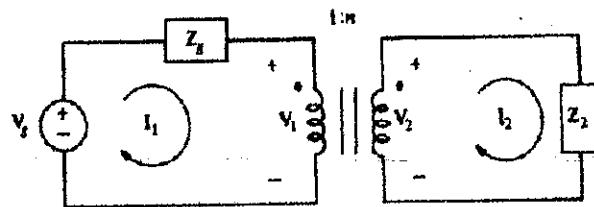


科目： 基礎電路學（電機系碩士在職專班）

共 | 頁 第 | 頁

電路學 每題 20 分

1. Find v and i of the following circuit.2. Find Thevenin equivalent circuit to the left of terminals a-b and find i .3. Find the steady-state current i .4. $V_g = 100\angle 0^\circ V$, $Z_g = 100\Omega$, and $Z_2 = 90k\Omega$. Find n such that $Z_1 = Z_g$, and then find the power delivered to Z_2 .5. Find the average power delivered to the 1Ω resistor.