

國立中山大學九十三年度碩士班招生考試試題

科目： 基礎電路學 (電機系碩士在職專班)

1. With the help of nodal analysis on the circuit of Fig.1, find (a)  $v_A$ ; (b) the power dissipated in the  $2.5\text{-}\Omega$  resistor. (15%)
2. If it is assumed that all the sources in the circuit of Fig.2 have been connected and operating for a very long time, use the superposition principle to find  $v_C(t)$  and  $v_L(t)$ . (15%)
3. (a) Find  $v_C(t)$  for  $t > 0$  in the circuit shown in Fig.3. (b) Sketch  $v_C(t)$  versus  $t$ ,  $-0.1 < t < 2$  ms. (15%)
4. For the network of Fig.4, find  $Z_{in}$  at  $\omega = 4$  rad/s if terminals a and b are (a) open-circuited; (b) short-circuited. (10%)
5. Use phasors and nodal analysis on the circuit of Fig.5 to find  $V_2$ . (15%)
6. Find the Thevenin-equivalent circuit for Fig.6. (15%)
7. (a) Write a set of mesh equations in terms of  $I_1(s)$ ,  $I_2(s)$ , and  $I_3(s)$  for the circuit shown in Fig.7. (b) Find  $I_3$  if  $s = -1$  Np/s. (15%)

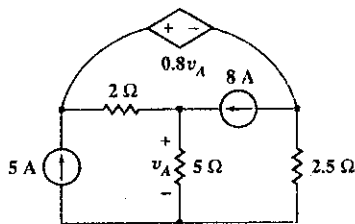


Figure 1.

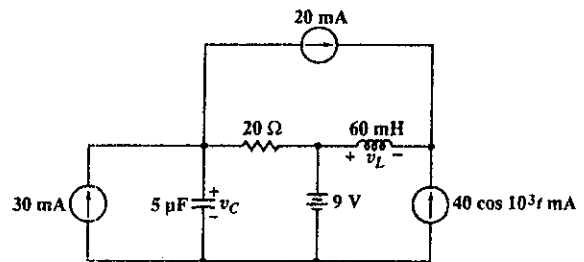


Figure 2.

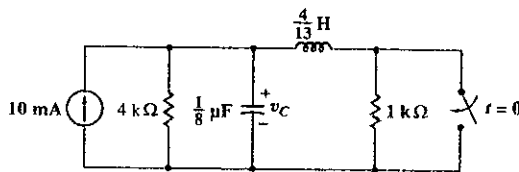


Figure 3.

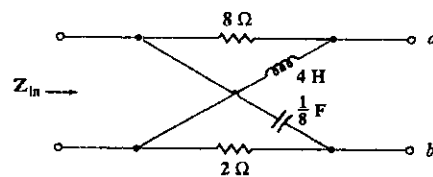


Figure 4.

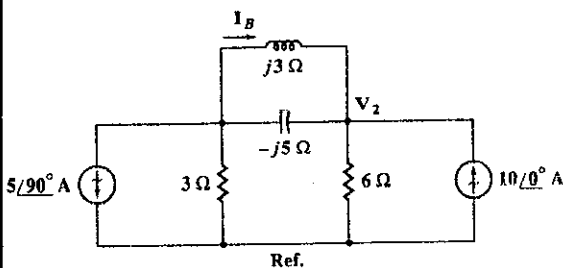


Figure 5.

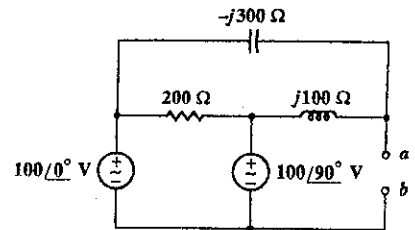


Figure 6.

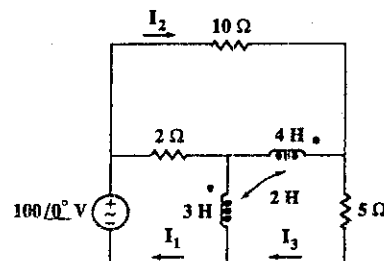


Figure 7.